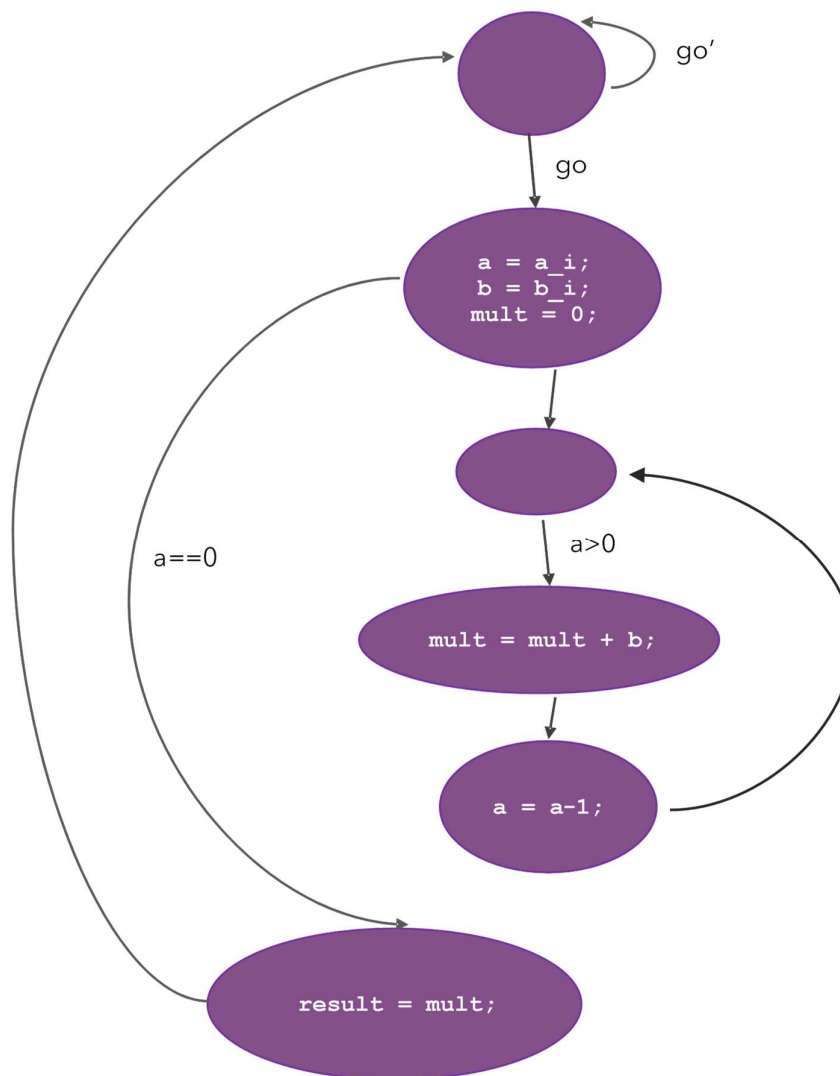


**GTU Department of Computer Engineering
CSE 232 - Spring 2020**

PROJECT 2 REPORT

**ESRA ERYILMAZ
171044046**

1. Decide states and draw the state diagram for your FSM controller.



- I get inputs (a_i and b_i) from user and return the multiplication result.
- User should also press "go" button once after entering the inputs.

(Since I used a single adder, I didn't put "mult = mult+b" and "a = a-1" with the same state.)



(I didn't need to write state for $a < 0$ because I made the signs positive at the beginning.)

Update FSM

(I accept '1' for signals written in the state , and for all the remaining signals '0'.)



2. Draw datapath.

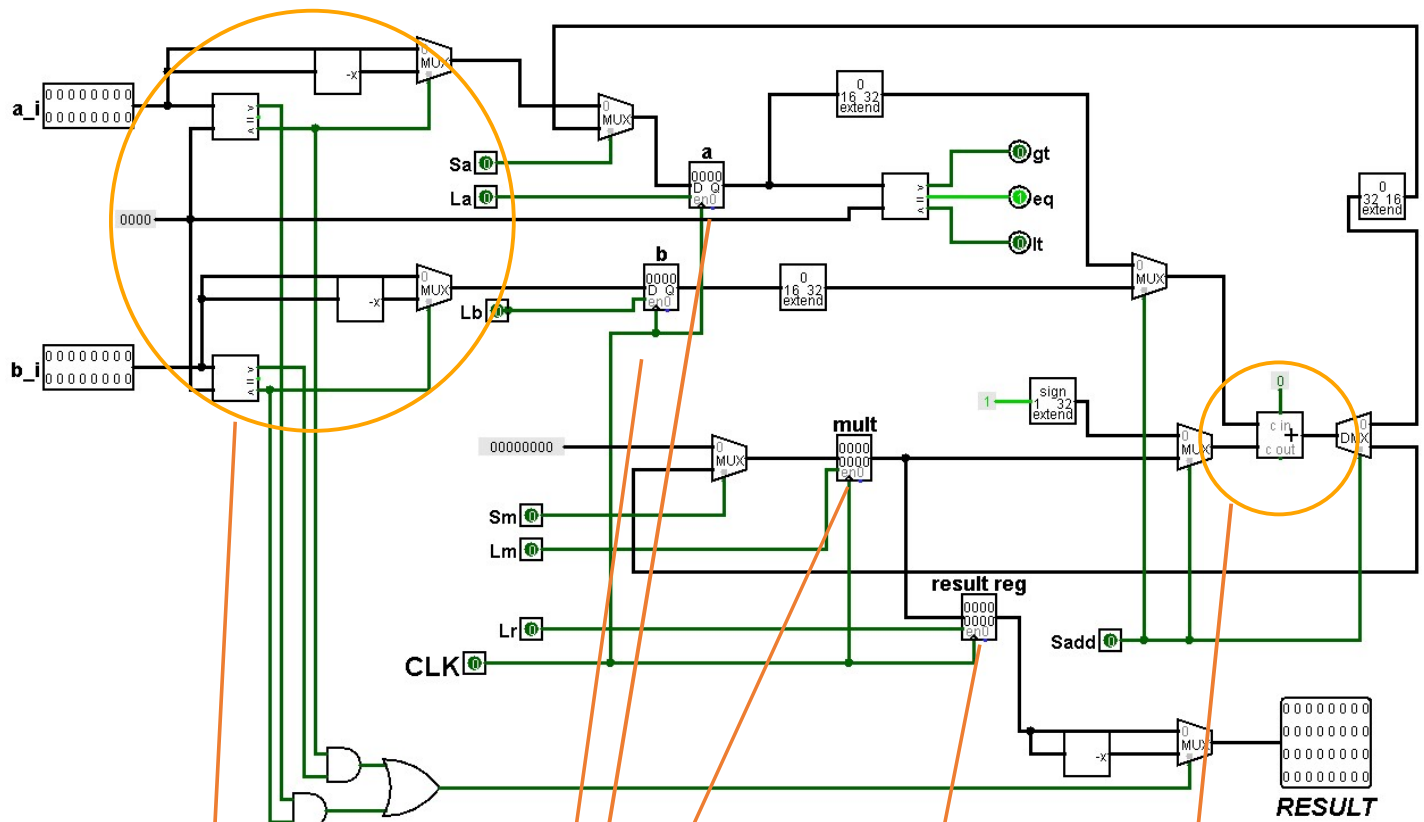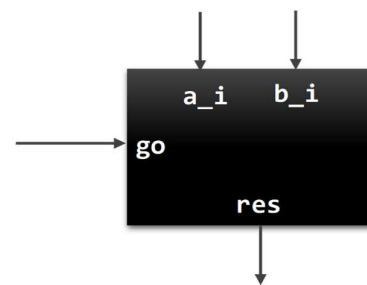

3. Draw truth table.

I have 6 states so 3 bit is enough.

Present States (PS)				Inputs			Next States (NS)		
	P2	P1	P0	gt	eq	go	N2	N1	N0
S0	0	0	0	-	-	0	0	0	0
	0	0	0	-	-	1	0	0	1
S1	0	0	1	-	-	-	0	1	0
S2	0	1	0	1	0	-	0	1	1
	0	1	0	0	1	-	1	0	1
S3	0	1	1	-	-	-	1	0	0
S4	1	0	0	-	-	-	0	1	0
S5	1	0	1	-	-	-	0	0	0

Outputs are just depends on states, so I showed it in separate truth table.

Present States (PS)				La	Lb	Lm	Sa	Sm	Sadd	Lr
	P2	P1	P0							
S0	0	0	0	0	0	0	0	0	0	0
S1	0	0	1	1	1	1	0	0	0	0
S2	0	1	0	0	0	0	0	0	0	0
S3	0	1	1	0	0	1	0	1	1	0
S4	1	0	0	1	0	0	1	0	0	0
S5	1	0	1	0	0	1	0	0	0	1

4. Derive Boolean expressions from the truth table.

$$N2 = P2' P1 P0' eq + P2' P1 P0$$

$$N1 = P2' P1' P0 + P2' P1 P0' gt + P2 P1' P0'$$

$$N0 = P2' P1' P0' go + P2' P1 P0' gt + P2' P1 P0' eq$$

$$La = S1 + S4$$

$$Lb = S1$$

$$Lm = S1 + S3 + S5$$



$$Sa = S4$$

$$Sm = S3$$


$$Sadd = S3$$

$$Lr = S5$$

5. Draw the circuit on Logisim.

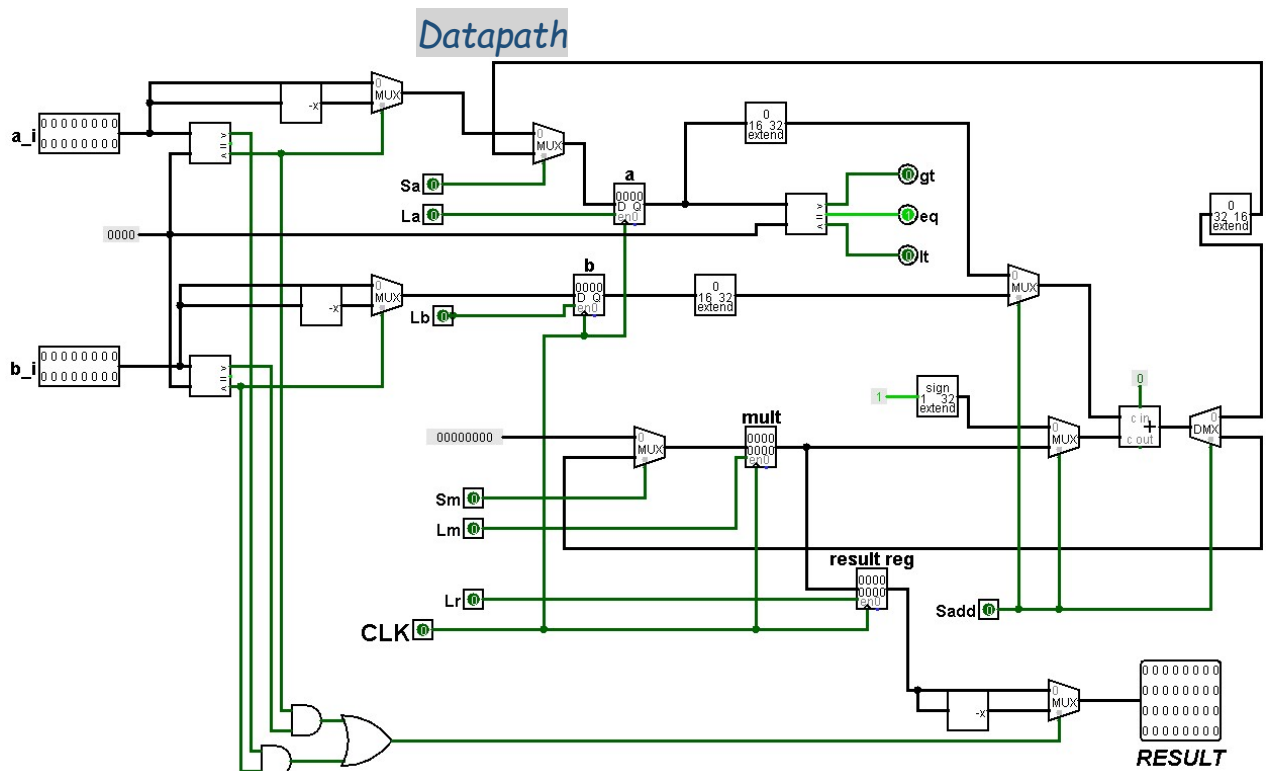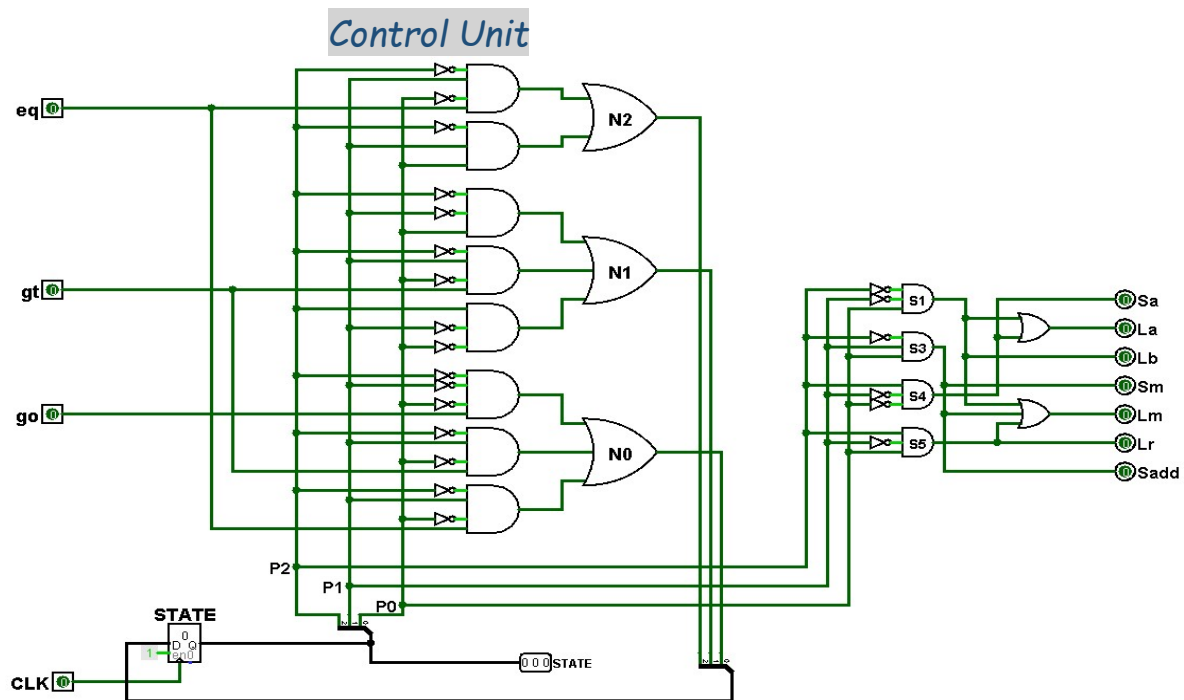

Main

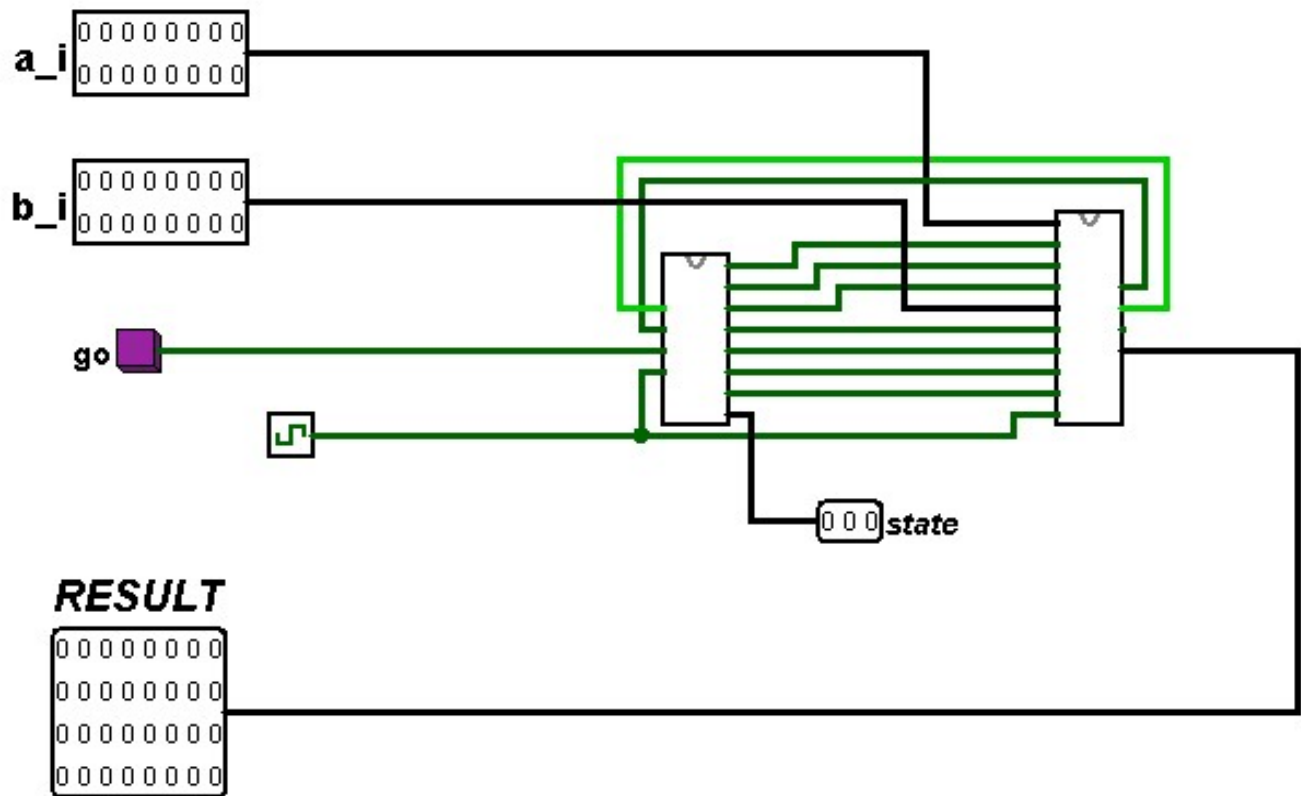

Optimizations

- Since I used a single adder, I connected double multiplexer to the input of the adder and I connected one demultiplexer to the output of the adder.
According to multiplexer select bit (`Sadd`), state machine decided which action to take.
- After taking the inputs, I check their signs and turn the negatives into positive.
- If the input signs are opposite, I return the result negative.
→ In this way, it works with negatives.

All parts are working.